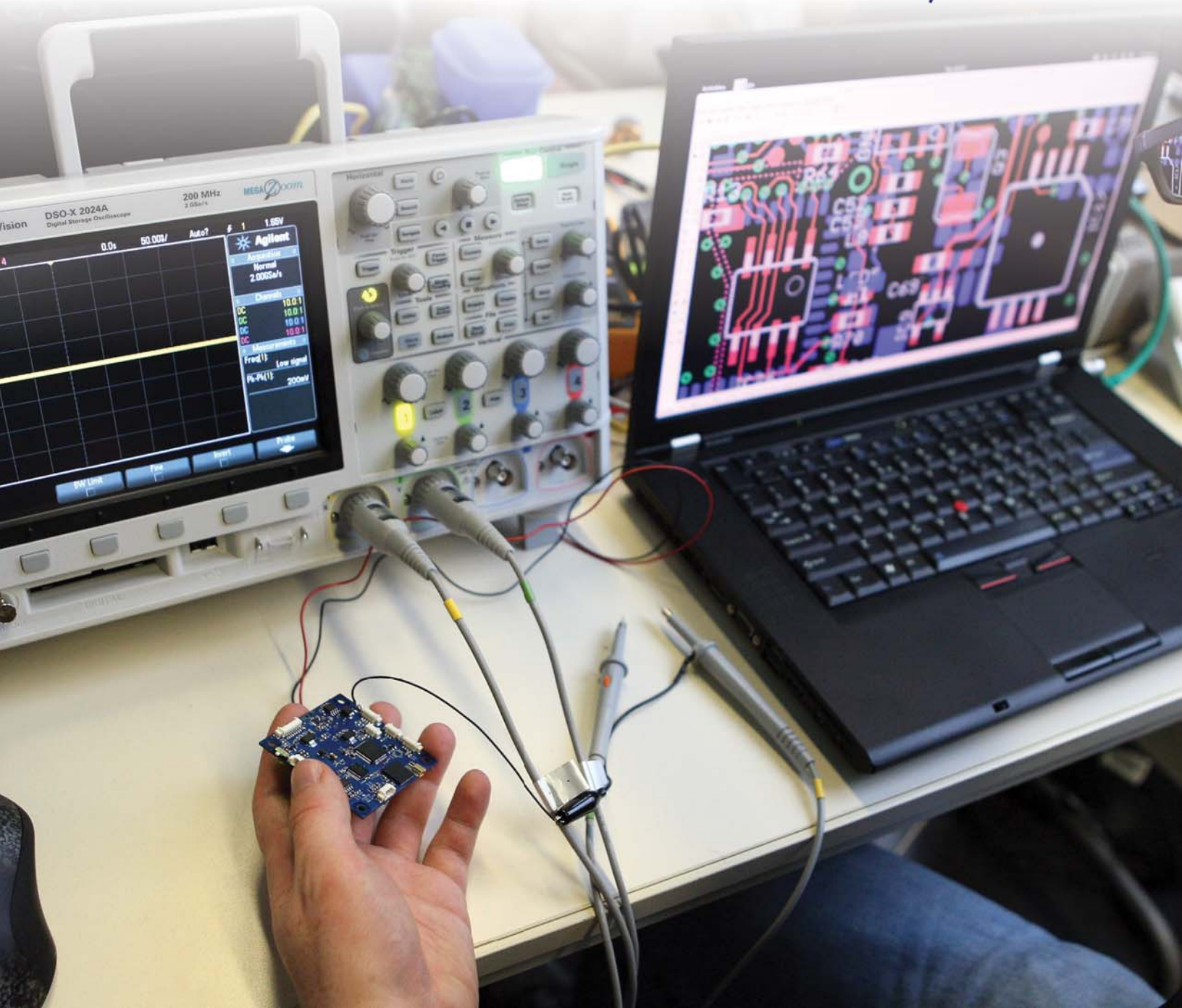


Contemporary Electronics

Fundamentals, Devices, Circuits, and Systems

Louis E. Frenzel, Jr.




Contemporary Electronics



Contemporary Electronics

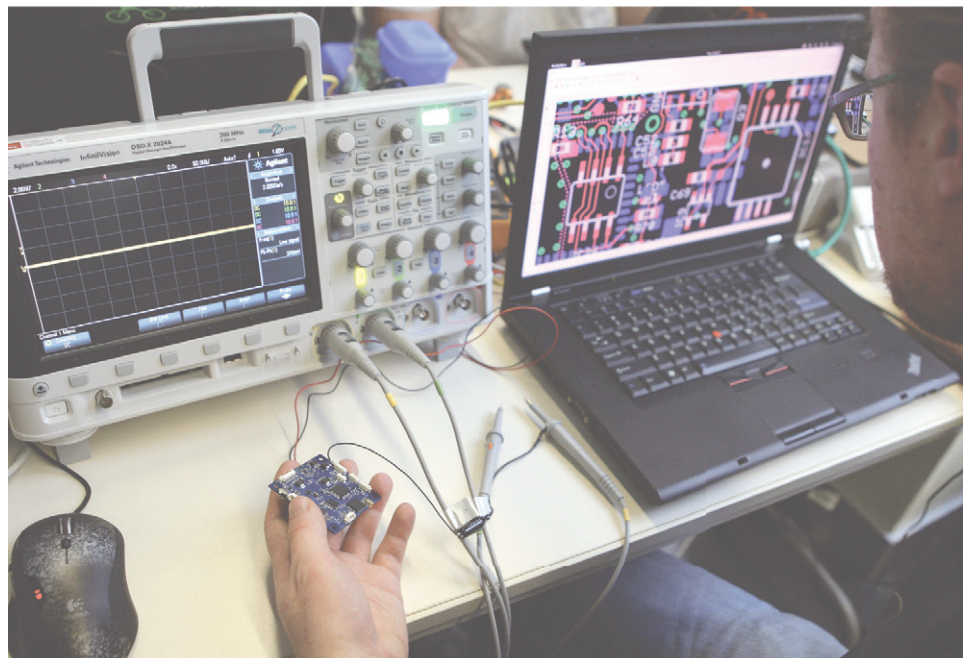Fundamentals, Devices, Circuits, and Systems



Louis E. Frenzel, Jr.





CONTEMPORARY ELECTRONICS: FUNDAMENTALS, DEVICES, CIRCUITS, AND SYSTEMS

Published by McGraw-Hill, a business unit of The McGraw-Hill Companies, Inc., 1221 Avenue of the Americas, New York, NY, 10020. Copyright © 2014 by The McGraw-Hill Companies, Inc. All rights reserved. Printed in the United States of America. No part of this publication may be reproduced or distributed in any form or by any means, or stored in a database or retrieval system, without the prior written consent of The McGraw-Hill Companies, Inc., including, but not limited to, in any network or other electronic storage or transmission, or broadcast for distance learning.

Some ancillaries, including electronic and print components, may not be available to customers outside the United States.

This book is printed on acid-free paper.

1 2 3 4 5 6 7 8 9 0 QVR/QVR 1 0 9 8 7 6 5 4 3

ISBN 978-0-07-337380-5

MHID 0-07-337380-X

Senior Vice President, Products & Markets: *Kurt L. Strand*
Vice President, General Manager, Products & Markets: *Martin J. Lange*
Vice President, Content Production & Technology Services: *Kimberly Meriwether David*
Managing Director: *Thomas Timp*
Director: *Michael D. Lange*
Executive Brand Manager: *Raghothaman Srinivasan*
Director of Development: *Rose Koos*
Development Editor: *Kelly H. Lowery*
Executive Marketing Manager: *Curt Reynolds*
Project Manager: *Jean R. Starr*
Senior Buyer: *Carol A. Bielski*
Lead Designer: *Matthew Baldwin*
Cover/Interior Designer: *Matthew Baldwin*
Cover Image: © *Getty Images*
Content Licensing Specialist: *Shawntel Schmitt*
Photo Researcher: *Colleen Miller*
Media Project Manager: *Cathy L. Tepper*
Typeface: *11/13 Times*
Compositor: *MPS Limited*
Printer: *Quad/Graphics*

All credits appearing on page or at the end of the book are considered to be an extension of the copyright page.

Library of Congress Cataloging-in-Publication Data

Cataloging-in-Publication Data has been requested from the Library of Congress.

The Internet addresses listed in the text were accurate at the time of publication. The inclusion of a website does not indicate an endorsement by the authors or McGraw-Hill, and McGraw-Hill does not guarantee the accuracy of the information presented at these sites.

To Joan with love for her help, support, and patience.

Brief Contents

Preface to the Instructor	xv	Chapter 17 Capacitive Circuits	282
Note to the Student	xvii	Chapter 18 Inductance and Transformers	295
Acknowledgments	xix	Chapter 19 Inductive Reactance	320
Walkthrough	xxi	Chapter 20 Inductive Circuits	329
PART 1			
Chapter 1 Survey of Electronics	1	Chapter 21 RC and L/R Time Constants	344
Chapter 2 Electricity	15	Chapter 22 Resonance	363
Chapter 3 Resistors	33	Chapter 23 Filters	381
Chapter 4 Ohm's Law	46	Chapter 24 AC Power	401
Chapter 5 Series Circuits	59	Chapter 25 Cables and Transmission Lines	427
Chapter 6 Parallel Circuits	76	Chapter 26 AC Testing and Troubleshooting	449
Chapter 7 Series-Parallel Circuits and Voltage Dividers	89	PART 3	
Chapter 8 Network Theorems	109	Chapter 27 A Systems Overview of Electronics	469
Chapter 9 Conductors, Insulators, and Semiconductors	127	Chapter 28 Semiconductors	486
Chapter 10 Batteries	145	Chapter 29 Diode Types and Operation	501
Chapter 11 Magnetism	165	Chapter 30 Power Supply Circuits	522
Chapter 12 DC Testing with Analog and Digital Multimeters	191	Chapter 31 Introduction to Transistors	544
Chapter 13 DC Troubleshooting	211	Chapter 32 Field-Effect Transistors, Amplifiers, and Switches	552
PART 2			
Chapter 14 Alternating Voltage and Current	232	Chapter 33 Bipolar Junction Transistors	579
Chapter 15 Capacitance	257	Chapter 34 Amplifier Fundamentals	618
Chapter 16 Capacitive Reactance	273	Chapter 35 Operational Amplifiers	638
		Chapter 36 Op-Amp Applications	665

Chapter 37	Power Amplifiers	693	Chapter 40	Thyristors	769
Chapter 38	Oscillators and Frequency Synthesizers	712	Chapter 41	Electronic System Troubleshooting	784
Chapter 39	Regulated Power Supplies and Power Conversion	744		Photo Credits805
				Index807

Contents

Preface to the Instructor	xv
Note to the Student	xvii
Acknowledgments	xix
Walkthrough	xxi

PART 1

Chapter 1 Survey of Electronics 1

1.1	Life Impact	2
1.2	Major Segments of the Electronics Industry	2
1.3	A Converged Industry	4
1.4	Jobs and Careers in the Electronics Industry	4
1.5	Engineering and Technology Education	6
1.6	The Major Employers	9
1.7	Where Are You Headed?	10
1.8	How Electronic Equipment and Circuits Work	11
1.9	An Electrical View of Electronics	12

Chapter 2 Electricity 15

2.1	Negative and Positive Polarities	16
2.2	Electrons and Protons in the Atom	16
2.3	Structure of the Atom	18
2.4	The Coulomb Unit of Electric Charge	19
2.5	The Volt Unit of Potential Difference	21
2.6	Charge in Motion Is Current	22
2.7	Resistance Is Opposition to Current	24
2.8	The Closed Circuit	25
2.9	The Direction of Current	26
2.10	Direct Current (DC) and Alternating Current (AC)	27
2.11	Sources of Electricity	28
2.12	The Digital Multimeter	29
	System Sidebar: A Solar-Powered Home Electrical System	30

Chapter 3 Resistors 33

3.1	Types of Resistors	34
3.2	Resistor Color Coding	37
3.3	Variable Resistors	40
3.4	Rheostats and Potentiometers	40

3.5	Power Rating of Resistors	42
	System Sidebar: Memristors	42

Chapter 4 Ohm's Law 46

4.1	The Current $I = V/R$	47
4.2	The Voltage $V = IR$	48
4.3	The Resistance $R = V/I$	48
4.4	Practical Units	49
4.5	Multiple and Submultiple Units	49
4.6	The Linear Proportion between V and I	50
4.7	Electric Power	51
4.8	Power Dissipation in Resistance	52
4.9	Power Formulas	53
	System Sidebar: The Binary Number System	54

Chapter 5 Series Circuits 59

5.1	Why I Is the Same in All Parts of a Series Circuit	60
5.2	Total R Equals the Sum of All Series Resistances	61
5.3	Series IR Voltage Drops	62
5.4	Kirchhoff's Voltage Law (KVL)	63
5.5	Polarity of IR Voltage Drops	64
5.6	Total Power in a Series Circuit	64
5.7	Series-Aiding and Series-Opposing Voltages	65
5.8	Analyzing Series Circuits with Random Unknowns	65
5.9	Ground Connections in Electrical and Electronic Systems	67
	System Sidebar: Light-Emitting Diodes	69

Chapter 6 Parallel Circuits 76

6.1	The Applied Voltage V_A Is the Same across Parallel Branches	77
6.2	Each Branch I Equals V_A/R	77
6.3	Kirchhoff's Current Law (KCL)	78
6.4	Resistances in Parallel	79
6.5	Conductances in Parallel	82
6.6	Total Power in Parallel Circuits	83

6.7	Analyzing Parallel Circuits with Random Unknowns	83
	System Sidebar: Christmas Lights	84

Chapter 7 Series-Parallel Circuits and Voltage Dividers 89

7.1	Finding R_T for Series-Parallel Resistances	90
7.2	Resistance Strings in Parallel	90
7.3	Resistance Banks in Series	92
7.4	Resistance Banks and Strings in Series Parallel	92
7.5	Analyzing Series-Parallel Circuits with Random Unknowns	93
7.6	The Wheatstone Bridge	95
7.7	Series Voltage Dividers	97
7.8	Series Voltage Divider with Parallel Load Current	99
	System Sidebar: Analyzing Circuits with Simulation Software	100

Chapter 8 Network Theorems 109

8.1	Kirchhoff's Current Law (KCL)	110
8.2	Kirchhoff's Voltage Law (KVL)	111
8.3	Thevenin's Theorem	113
8.4	Thevenizing a Bridge Circuit	115
8.5	Voltage Sources	116
8.6	Maximum Power Transfer Theorem	118
	System Sidebar: Digital-to-Analog Converter	119

Chapter 9 Conductors, Insulators, and Semiconductors 127

9.1	Function of the Conductor	128
9.2	Standard Wire Gage Sizes	128
9.3	Types of Wire Conductors	130
9.4	Connectors	131
9.5	Printed Wiring	131
9.6	Switches	132
9.7	Fuses	134
9.8	Wire Resistance	135
9.9	Temperature Coefficient of Resistance	136
9.10	Resistive Sensors	136
9.11	Insulators	139
9.12	Semiconductors	139
	System Sidebar: Lightbulbs	140

Chapter 10 Batteries 145

10.1	Introduction to Batteries	146
10.2	The Voltaic Cell	147
10.3	Common Types of Primary Cells	148

10.4	Lead-Acid Wet Cell	150
10.5	Additional Types of Secondary Cells	152
10.6	Series-Connected and Parallel-Connected Cells	154
10.7	Current Drain Depends on Load Resistance	156
10.8	Internal Resistance of a Generator	157
10.9	Constant-Voltage and Constant-Current Sources	158
	System Sidebar: Battery Charging	159

Chapter 11 Magnetism 165

11.1	The Magnetic Field	166
11.2	Magnetic Units of Measurement	167
11.3	Induction by the Magnetic Field	168
11.4	Types of Magnets	169
11.5	Magnetic Shielding	171
11.6	The Hall Effect	171
11.7	Ampere-Turns of Magnetomotive Force (mmf)	172
11.8	Field Intensity (H)	172
11.9	B - H Magnetization Curve	173
11.10	Magnetic Hysteresis	174
11.11	Magnetic Field around an Electric Current	175
11.12	Magnetic Polarity of a Coil	176
11.13	Motor Action between Two Magnetic Fields	177
11.14	Induced Current	178
11.15	Generating an Induced Voltage	180
11.16	Relays	181
	System Sidebar: DC Motors	184

Chapter 12 DC Testing with Analog and Digital Multimeters 191

12.1	Moving-Coil Meter	192
12.2	Meter Shunts	193
12.3	Voltmeters	195
12.4	Loading Effect of a Voltmeter	197
12.5	Ohmmeters	198
12.6	Multimeters	200
12.7	Digital Multimeter (DMM)	201
12.8	Meter Applications	202
12.9	Checking Continuity with the Ohmmeter	203
12.10	Alternating Current Measurements	204
	System Sidebar: Data Acquisition System	204

Chapter 13 DC Troubleshooting 211

13.1	Introduction to Troubleshooting	212
13.2	Resistor Troubles	212
13.3	Open-Circuit and Short-Circuit Troubles	213
13.4	Troubleshooting: Opens and Shorts in Series Circuits	213

13.5	Troubleshooting: Opens and Shorts in Parallel Circuits	216
13.6	Troubleshooting: Opens and Shorts in Series-Parallel Circuits	220
13.7	Troubleshooting Hints for Wires and Connectors	223
13.8	Troubleshooting a DC System	223
	System Sidebar: DC Power System	224

PART 2

Chapter 14 Alternating Voltage and Current 232

14.1	Alternating Current Applications	233
14.2	Alternating-Voltage Generator	233
14.3	The Sine Wave	235
14.4	Alternating Current	236
14.5	Voltage and Current Values for a Sine Wave	237
14.6	Frequency	238
14.7	Period	239
14.8	Wavelength	239
14.9	Phase Angle	241
14.10	The Time Factor in Frequency and Phase	243
14.11	Alternating Current Circuits with Resistance	243
14.12	Nonsinusoidal AC and DC Waveforms	244
14.13	The Frequency Domain and the Fourier Theory	246
	System Sidebar: The Frequency Spectrum	251

Chapter 15 Capacitance 257

15.1	How Charge Is Stored in a Dielectric	258
15.2	Charging and Discharging a Capacitor	258
15.3	The Farad Unit of Capacitance	260
15.4	Typical Capacitors	262
15.5	Electrolytic Capacitors	265
15.6	Supercapacitors	266
15.7	Stray and Distributed Capacitance	267
15.8	Parallel Capacitances	268
15.9	Series Capacitances	268
	System Sidebar: Dynamic Random Access Memory	269

Chapter 16 Capacitive Reactance 273

16.1	Alternating Current in a Capacitive Circuit	274
16.2	The Amount of X_C Equals $1/(2\pi fC)$	275
16.3	Series or Parallel Capacitive Reactances	276
16.4	Ohm's Law Applied to X_C	277
16.5	Sine-Wave Charge and Discharge Current	277

Chapter 17 Capacitive Circuits 282

17.1	Sine Wave v_C Lags i_C by 90°	283
17.2	X_C and R in Series	284
17.3	Impedance Z Triangle	285
17.4	RC Phase-Shifter Circuit	286
17.5	X_C and R in Parallel	287
17.6	RF and AF Coupling Capacitors	290
17.7	Capacitive Voltage Dividers	290

Chapter 18 Inductance and Transformers 295

18.1	Induction by Alternating Current	296
18.2	Self-Inductance L	296
18.3	Self-Induced Voltage v_L	298
18.4	How v_L Opposes a Change in Current	299
18.5	Mutual Inductance L_M	300
18.6	Transformers	301
18.7	Transformer Ratings	305
18.8	Impedance Transformation	307
18.9	Core Losses	309
18.10	Types of Cores	309
18.11	Variable Inductance	310
18.12	Inductances in Series or Parallel	311
18.13	Stray Capacitive and Inductive Effects	312
	System Sidebar: AC Motors	314

Chapter 19 Inductive Reactance 320

19.1	How X_L Reduces the Amount of I	321
19.2	$X_L = 2\pi fL$	322
19.3	Series or Parallel Inductive Reactances	324
19.4	Ohm's Law Applied to X_L	324
19.5	Applications of X_L for Different Frequencies	325
19.6	Waveshape of v_L Induced by Sine-Wave Current	325

Chapter 20 Inductive Circuits 329

20.1	Sine Wave i_L Lags v_L by 90°	330
20.2	X_L and R in Series	330
20.3	Impedance Z Triangle	332
20.4	X_L and R in Parallel	333
20.5	Q of a Coil	335
20.6	AF and RF Chokes	336
20.7	Power in AC Circuits	337
20.8	Complex Impedances	338
	System Sidebar: Power Factor Correction	339

Chapter 21 RC and L/R Time Constants 344

21.1	Response of Resistance Alone	345
21.2	L/R Time Constant	345

21.3	High Voltage Produced by Opening an RL Circuit	346
21.4	RC Time Constant	346
21.5	RC Charge and Discharge Curves	348
21.6	High Current Produced by Short-Circuiting an RC Circuit.	349
21.7	RC Waveshapes	349
21.8	Long and Short Time Constants.	350
21.9	Charge and Discharge with a Short RC Time Constant	351
21.10	Long Time Constant for an RC Coupling Circuit.	352
21.11	Advanced Time Constant Analysis	352
	System Sidebar: Data Rate vs. Bandwidth	355

Chapter 22 Resonance 363

22.1	The Resonance Effect	364
22.2	Series Resonance	364
22.3	Parallel Resonance	366
22.4	Resonant Frequency $f_r = 1/(2\pi\sqrt{LC})$	368
22.5	Q Magnification Factor of a Resonant Circuit.	370
22.6	Bandwidth of a Resonant Circuit	373
22.7	Tuning.	375
22.8	Damping of Parallel Resonant Circuits	376

Chapter 23 Filters 381

23.1	Ideal Responses	382
23.2	Filter Circuits	384
23.3	Low-Pass Filters	384
23.4	High-Pass Filters	385
23.5	Analyzing Filter Circuits	386
23.6	Decibels and Frequency Response Curves.	389
23.7	Resonant Filters	394
23.8	Special Filter Types	395
	System Sidebar: DSP Filters	396

Chapter 24 AC Power 401

24.1	Power Generation	402
24.2	Power Distribution	405
24.3	Home Electric Wiring	409
24.4	Three-phase AC Power.	413
24.5	Wires, Cables, and Components.	414
24.6	Electrical Safety	415
24.7	Alternative Energy	419
	System Sidebar: The Smart Grid.	423

Chapter 25 Cables and Transmission Lines 427

25.1	Cables vs. Transmission Lines	428
25.2	Principles of Transmission Lines	428

25.3	Transmission Line Specifications and Characteristics	431
25.4	How a Transmission Line Works	434
25.5	Twisted Pair Cables	437
25.6	Coaxial Cable.	441
	System Sidebar: Fiber-Optic Cable and Its Application	445

Chapter 26 AC Testing and Troubleshooting 449

26.1	Introduction to the Oscilloscope	450
26.2	Analog Oscilloscopes.	451
26.3	Oscilloscope Probes	453
26.4	Digital Oscilloscopes	454
26.5	Voltage and Time Measurements.	457
26.6	Function Generators	460
26.7	Virtual Instruments	461
26.8	AC Testing and Troubleshooting Examples	463

PART 3

Chapter 27 A Systems Overview of Electronics 469

27.1	Introduction to Systems	470
27.2	How Circuits and Systems Work	472
27.3	Linear, or Analog, Circuits.	472
27.4	Digital Circuits	476
27.5	Interface or Mixed Signal Circuits.	479
27.6	System Examples	479

Chapter 28 Semiconductors 486

28.1	Conductors	487
28.2	Semiconductors	487
28.3	Silicon Crystals	488
28.4	Intrinsic Semiconductors	490
28.5	Two Types of Flow	491
28.6	Doping a Semiconductor	491
28.7	Two Types of Extrinsic Semiconductors	492
28.8	The Unbiased Diode.	492
28.9	Forward Bias	493
28.10	Reverse Bias	494
28.11	Breakdown	495
28.12	Advances in Semiconductors	496

Chapter 29 Diode Types and Operation 501

29.1	Basic Diode Characteristics	502
29.2	The Ideal Diode	503
29.3	The Second and Third Approximations.	505
29.4	Key Diode Specifications	506

29.5	DC Resistance of a Diode	507
29.6	Surface-Mount Diodes	507
29.7	The Zener Diode	507
29.8	The Loaded Zener Regulator	509
29.9	Zener Specifications	511
29.10	Optoelectronic Devices	511
29.11	The Schottky Diode	514
29.12	The Varactor	515
29.13	Other Diodes	517

Chapter 30 Power Supply Circuits 522

30.1	The Power Supply Subsystem	523
30.2	The Half-Wave Rectifier	524
30.3	The Transformer	525
30.4	The Full-Wave Rectifier	526
30.5	The Bridge Rectifier	527
30.6	Power Supply Filtering	529
30.7	Peak Inverse Voltage and Surge Current	534
30.8	Other Power Supply Topics	535
30.9	Troubleshooting	536
30.10	Voltage Multipliers	537

Chapter 31 Introduction to Transistors 544

31.1	The Concept of a Transistor	545
31.2	The Transistor as a Switch	545
31.3	The Transistor as an Amplifier	548
31.4	Types of Transistors	549

Chapter 32 Field-Effect Transistors, Amplifiers, and Switches 552

32.1	Introduction to FETs	553
32.2	Junction FET Basics	553
32.3	Drain Curves	554
32.4	The Transconductance Curve	555
32.5	Biasing the JFET	556
32.6	Transconductance	557
32.7	JFET Amplifiers	558
32.8	Special Types of JFETs	559
32.9	The Depletion-Mode MOSFET	559
32.10	D-MOSFET Curves	560
32.11	Depletion-Mode MOSFET Amplifiers	561
32.12	The Enhancement-Mode MOSFET	562
32.13	The Ohmic Region	564
32.14	Digital Switching	565
32.15	CMOS	567
32.16	Power FETs	567
32.17	E-MOSFET Amplifiers	570
32.18	Differential Amplifiers	571
32.19	MOSFET Circuits and Static Electricity	573

Chapter 33 Bipolar Junction Transistors 579

33.1	The Unbiased Transistor	580
33.2	The Biased Transistor	580
33.3	Transistor Currents	581
33.4	The CE Connection	582
33.5	The Base Curve	583
33.6	Collector Curves	584
33.7	Reading Data Sheets	586
33.8	Surface-Mount Transistors	588
33.9	Basic Biasing	588
33.10	Emitter Bias	589
33.11	Voltage Divider Bias	590
33.12	Troubleshooting Transistor Circuits	592
33.13	PNP Transistors	592
33.14	Typical Bipolar Amplifiers	593
33.15	Emitter Follower	596
33.16	The Differential Amplifier	600
33.17	The Transistor Switch	605
33.18	Driver Circuits	606
33.19	Special Bipolar Transistors	607

Chapter 34 Amplifier Fundamentals 618

34.1	Types of Amplifiers	619
34.2	Frequency Response of an Amplifier	619
34.3	Decibel Power Gain	621
34.4	Decibel Voltage Gain	622
34.5	Impedance Matching	624
34.6	Decibels above a Reference	627
34.7	Bode Plots	628
34.8	More Bode Plots	630
34.9	Rise Time–Bandwidth Relationship	633
34.10	Frequency Effects of Surface-Mount Circuits	634

Chapter 35 Operational Amplifiers 638

35.1	Introduction to Op Amps	639
35.2	The 741 Op Amp	640
35.3	The Inverting Amplifier	645
35.4	The Noninverting Amplifier	648
35.5	Common Op-Amp Applications	650
35.6	Op Amps as Surface-Mount Devices	652
35.7	Differential Amplifiers	652
35.8	Instrumentation Amplifiers	655
35.9	Single-Supply Operation	656
System Sidebar: Balanced and Unbalanced Signal Wiring in Electronic Systems		657

Chapter 36 Op-Amp Applications 665

36.1	Comparators with Zero Reference	666
36.2	Comparators with Nonzero References	669
36.3	Comparators with Hysteresis	672

36.4	The Integrator	674
36.5	Waveform Conversion	675
36.6	Waveform Generation	677
36.7	Active Diode Circuits	679
36.8	Active Filters	679
36.9	First-Order Stages	679
36.10	Second-Order Low-Pass Filters	682
36.11	High-Pass Filters	682
36.12	Higher-Order Filters and Filter Design	682
36.13	Bandpass Filters	683
36.14	Bandstop Filters	684
36.15	The All-Pass Filter	685
	System Sidebar: Video Surveillance	686

Chapter 37 Power Amplifiers 693

37.1	Amplifier Terms	694
37.2	Class A Operation	694
37.3	Class B Operation	698
37.4	Class B Push-Pull Emitter Follower	699
37.5	Class C Operation	703
37.6	Switching Amplifiers	705
37.7	Transistor Power Rating	707
	System Sidebar: Class G and Class H Amplifiers	708

Chapter 38 Oscillators and Frequency Synthesizers 712

38.1	Theory of Sinusoidal Oscillation	713
38.2	The Wien-Bridge Oscillator	713
38.3	The Colpitts Oscillator	715
38.4	Other LC Oscillators	716
38.5	Quartz Crystals	718
38.6	Crystal Oscillators	719
38.7	Square-Wave, Pulse, and Function Generators	722
38.8	The Phase-Locked Loop	732

38.9	Frequency Synthesizers	734
	System Sidebar: The Concept of Modulation	736

Chapter 39 Regulated Power Supplies and Power Conversion 744

39.1	Power Supply Review	745
39.2	Supply Characteristics	745
39.3	Basic Regulators	746
39.4	Series Regulators	748
39.5	Linear IC Regulators	750
39.6	Introduction to Switch-Mode Power Supplies	754
39.7	Switching Regulators	756
39.8	DC-DC Converters	760
39.9	Inverters	763

Chapter 40 Thyristors 769

40.1	The Four-Layer Diode	770
40.2	The Silicon-Controlled Rectifier	771
40.3	The SCR Crowbar	774
40.4	SCR Phase Control	775
40.5	Bidirectional Thyristors	777
40.6	IGBTs	779
	System Sidebar: IGBT Switching Power Converters	780

Chapter 41 Electronic System Troubleshooting 784

41.1	Electronic Instrumentation	785
41.2	An Introduction to Troubleshooting	790
41.3	Circuit Troubleshooting	792
41.4	Power Supply Troubleshooting	794
41.5	Alternative Troubleshooting Techniques	795
41.6	Systems Troubleshooting	798

	Photo Credits	805
	Index	807